

Evaluation of Minterm Expression

Gaurav Prajapati

Contents

1	Problem	2
2	Introduction	2
3	Components	2
4	Solution	3
4.1	Karnaugh Map	3
4.2	Truth Table	3
5	Connections	4
5.1	LED to Arduino	4
5.2	Input Pins to Arduino	4
5.3	Setting Input Pin Values	4
6	Code	5
6.1	main.cpp	5
6.2	Repository	5

1 Problem

(GATE CS-2014 SET-3)

Q.7 Consider the Following Minterm expression for F:

$$F(P, Q, R, S) = \sum 0, 2, 5, 7, 8, 10, 13, 15$$

The minterms 2,7,8 and 13 are '*do not care*' terms. The minimal sum-of-products form for F is

- (A) $Q\bar{S} + \bar{Q}S$
- (B) $\bar{Q}\bar{S} + QS$
- (C) $\bar{Q}\bar{R}\bar{S} + \bar{Q}R\bar{S} + Q\bar{R}S + QRS$
- (D) $\bar{P}\bar{Q}\bar{S} + \bar{P}QS + PQS + P\bar{Q}\bar{S}$

2 Introduction

For a given set of Boolean Logic Inputs, we can define the following terms:

- **Minterm** is a boolean expression resulting in an output of 1 for the minimum number of cells in a Karnaugh-Map (K-Map) and 0 in other cells.
- **Sum of Products** is a boolean expression for the *Sum* (OR) of various *Product* (AND) terms.
- '**do not care**' terms for a boolean expression are the set of input values for which the output of the function does not matter. The value for these can be taken as 0 or 1 by choice

3 Components

Component	Value	Quantity
Arduino	UNO	1
Breadboard	-	1
LED	-	1
Jumper Wires	M-M	10
Resistor	220 Ω	1

Table 1: Table of Components

4 Solution

4.1 Karnaugh Map

$$F(P, Q, R, S) = \sum(0, 2, 5, 7, 8, 10, 13, 15) + d(2, 7, 8, 13)$$

		<i>PQ</i>			
		00	01	11	10
<i>RS</i>	00	1	0	0	X
	01	0	1	X	0
	11	0	X	1	0
	10	X	0	0	1

The above K-Map can be simplified to:

$$F = \bar{Q} \cdot \bar{S} + Q \cdot S \quad (1)$$

Therefore, the answer is **(A)**

4.2 Truth Table

P	Q	R	S	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Table 2: Truth Table for F

5 Connections

5.1 LED to Arduino

LED connections to Arduino are as follows:

Arduino	2	GND
LED	+	-

Table 3: LED Connections

5.2 Input Pins to Arduino

Input Pin Connections to Arduino are as follows:

Arduino	D6	D7	D8	D9
Term	P	Q	R	S

Table 4: Input Pin Connections

5.3 Setting Input Pin Values

The values of the Input pins are taken by connecting them to either 5V or GND according to Truth Table

6 Code

6.1 main.cpp

The Arduino implementation uses the following code:

```
1 // Required for Arduino
2 #include "Arduino.h"
3
4 // Declaring variables
5 byte P,Q,R,S,F;
6
7 void setup()
8 {
9     // Output Pins
10    pinMode(2, OUTPUT);
11
12    // Input Pins
13    pinMode(6, INPUT);
14    pinMode(7, INPUT);
15    pinMode(8, INPUT);
16    pinMode(9, INPUT);
17 }
18
19 void loop()
20 {
21     // Reading P,Q,R,S
22     P = digitalRead(6);
23     Q = digitalRead(7);
24     R = digitalRead(8);
25     S = digitalRead(9);
26
27     //  $F(P,Q,R,S) = Q'.S' + Q.S$ 
28     F = (Q && S) || (!Q && !S);
29
30     // Setting Pin 2 to F
31     digitalWrite(2, F);
32 }
```

6.2 Repository

Code is also available online at the following repository:

<https://github.com/gaurav5-5/ard-workshop/tree/main/ide/latex/codes>